

DIM MODE SIGNAL:

Specification:

This component will produce a signal that will reflect the clock. By having it tied to the clock, it produces a 50% duty cycle signal. The result after going through the LED in later components will produce a dimmer signal due to being on only half the time.

Inputs:

Clock: CLK

Outputs:

Single wire tied to the clock

Schematic:

DIM MODE SIGNAL

CLK ——— OUT

Performance:

A wire tied to the clock.

Total GIE: 0